

Example 2– Revisit Capacitor Part 1, Ex 2

A 12.47 kV wye-connected three-phase feeder serves a mix of residential and commercial load as shown below with three-phase peak loading values as follows:

<u>Section #</u>	<u>Load Type</u>	<u>Load (kVA)</u>	<u>P.F. (lagging)</u>	<u>Line Length (miles)</u>
0-1	Spot	2000	0.9	1.5
1-2	Spot	2000	0.9	1.5
2-3	Spot	1000	0.9	1.0
3-4	Spot	1500	0.9	2.0


The feeder consists of 336 conductors with positive sequence impedances of:

$R = 0.306$ Ohms/phase-miles and $X = 0.630$ Ohms/phase-miles.

The substation voltage at Bus 0 is regulated at 1.04 p.u. Use the K factor approach to calculate the voltages requested below.

- (c) Now we want to evaluate adding a Capacitor to improve the circuit using the $\frac{1}{2}$ kVAR rule. Starting with no capacitor in the circuit, then add a 2700 kVAR capacitor bank to Bus 2.
- Determine the new voltage at Bus 4.
 - Determine the new value for circuit kW losses.
- (d) Which capacitor placement gives better results in terms of reducing circuit kW losses?

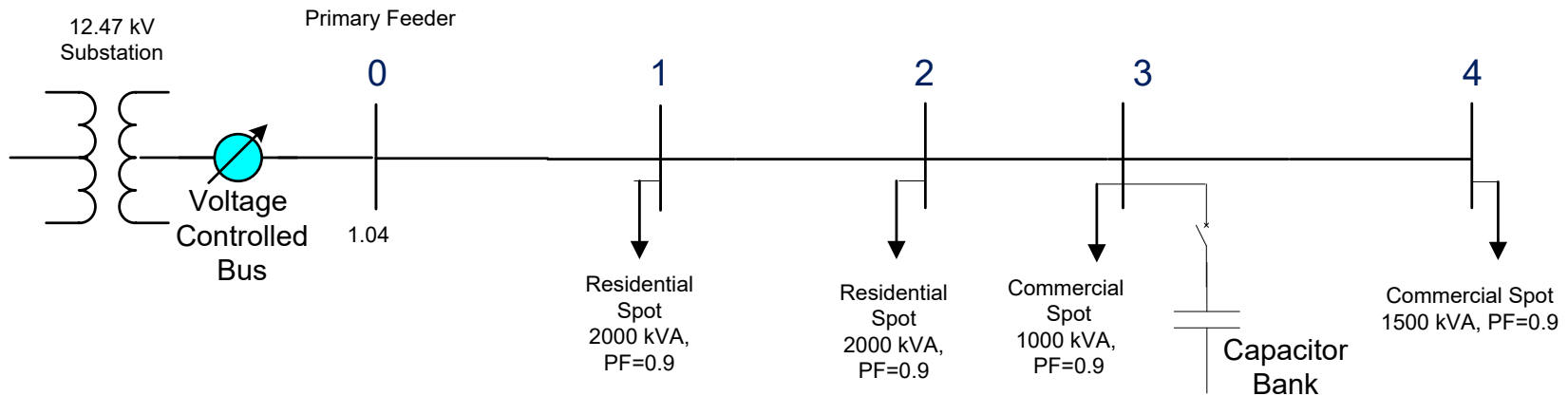Example 2 – Fixed Capacitor Bank Sizing (2)



Feeder Diagram for Capacitor Sizing Problem

Example 2 – Section Q Flows

(c) Adding cap banks using $1/2$ kWAr rule.

Condition imp to 1.0 pf.

Location & Size :-

$$\text{Total reactive power} = 6500 * \sin(25.84) = 2833.3 \text{ kWAr}$$

We have 300 kWAr (3φ) cap banks.

$$\Rightarrow \text{number of cap banks required} = \frac{2833.3}{300} = 9.4 \sim "9" \text{ cap banks}$$

$$\Rightarrow 1/2 \text{ Cap. Var rating} = \left(\frac{1}{2} * 2700 = 1350 \text{ kWAr} \right)$$

$$Q_{01} = 6500 * \sin(25.84) = 2833.3 \text{ kWAr}$$

$$Q_{12} = 4500 * \sin(25.84) = 1961.36 \text{ kWAr}$$

$$Q_{23} = 2500 * \sin(25.84) = 1089.65 \text{ kWAr}$$

$$Q_{34} = 1500 * \sin(25.84) = 653.8 \text{ kWAr}$$

Thus based on the data obtained

The best location for the Cap. bank location is bus 2.



Example 2 - 1/2 kVAR Rule – Voltage Drops

$$\Delta VD_{\phi_1} = 1.5 [-4.051 \times 10^{-4}] * 2700 = -1.64 \text{ percent (\%.)}$$

$$\Delta VD_{12}^{\text{cap}} = 1.5 [-4.051 \times 10^{-4}] * 2700 = -1.64 \%$$

$$\Rightarrow V_4 = 1.04 - \left(\frac{7.785}{100} \right) + \left(\frac{1.64}{100} \right) * 2 = 0.995 \text{ per unit} \quad \underline{\underline{\text{or } 7164 \text{ volts}}}$$

$$Q_{\phi_1} = (2833.3 - 2700) \text{ kVAR} = 133.3 \text{ kVAR}$$

$$P_{\phi_1} = 6500 * 6 \sin(25.84) = 5850.09 \text{ kW}$$

$$\Rightarrow \text{new } S_{\phi_1} = 5851.6 \angle 1.30 \Rightarrow \cos(1.3) = 0.999 \quad \underline{\underline{\text{XXXXXXXXXXXX}}}$$

Thus, it's also clear that ~~the~~ addition of kVAR's via cap bank improves the top of feeder power factor.

Example 2 - ½ kVAR Rule – Current Flows and Losses

improves the top of feeder power factor.

$$ii) |I_{01}| = \frac{\sqrt{(6500 * 0.9)^2 + (2833 - 2700)^2}}{\sqrt{3} * 12.47} = 270.92 \text{ Amps.}$$

$$|I_{12}| = \frac{\sqrt{(4500 * 0.9)^2 + (1961 - 2700)^2}}{\sqrt{3} * 12.47} = 190.61 \text{ Amps.}$$

$$|I_{23}| = 115.75 \text{ Amps} \ \& \ |I_{34}| = 69.45 \text{ Amps} \left] \begin{array}{l} \text{previously} \\ \text{calculated.} \end{array} \right.$$

$$\begin{aligned} P_{Loss} &= 3 * (270.92)^2 * (0.306 * 1.5) + 3 * (190.61)^2 * (0.306 * 1.5) \\ &\quad + 3 * (115.75)^2 * (0.306) + 3 * (69.45)^2 * (0.306 * 2) \text{ PP10} \\ &= [(101.1) + (50.03) + (12.3) + (8.85)] \text{ kWatts} \\ &= \underline{\underline{172.3 \text{ kWatts}}} \end{aligned}$$

Example 2 - $\frac{1}{2}$ kVAR Rule - Comparison

- (d)
- Comparing two results we can see that losses are nearly same. But number of capacitors required in part 'B' is less than part 'C'.
 - Normally we see lower losses when we use $\frac{1}{2}$ kVAR rule but in systems under consideration we can observe that the Q injection is improving voltage profile of bus 1 & 2. as these buses are loaded more.
 - Cap. bank placement at bus 2 or bus 3 is ~~not~~ causing similar effects in the voltage profile and losses.